

Transfer Functions RLC Circuits - Part of Part 3.

Resource: Solutions & Problems of Control Systems, 2nd ed - AK Jairath.

My Homework. This is a pre-requisite study for Laplace Transforms in circuit analysis.


Source of study material: Electric Circuits 6th Ed., Nahvi & Edminister. Engineering Circuit Analysis, Hyatt & Kimmerly 4th Ed. McGrawHill. Karl S. Bogha.

Solved Problems In Transfer Functions of RLC circuits.

Resource: Solutions & Problems of Control Systems, 2nd ed - AK Jairath.

Level: Intermediate.

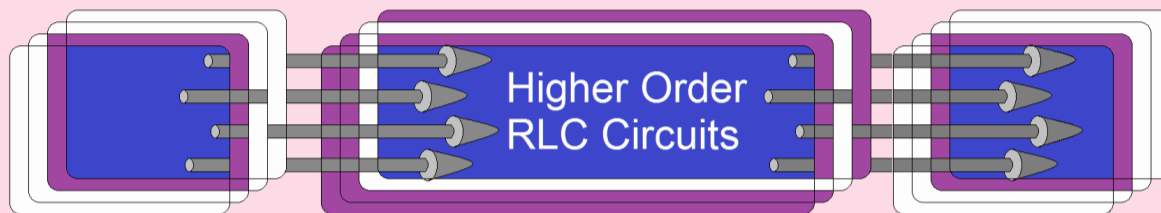Circuiting Prerequisites To Laplace Transform Electric Circuits.



Transfer Functions


(Intermediate Level)

Apologies for any errors and omissions.

August 2020.

Non-Commercial Use Only

Where the sL and $1/sC$ came from?

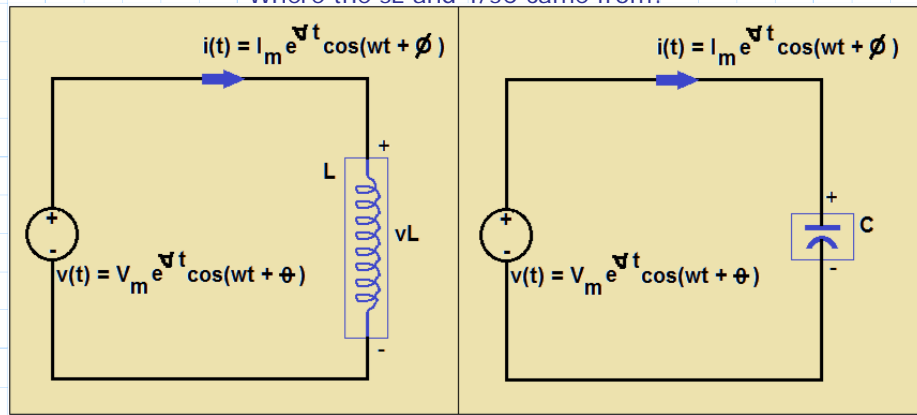

$$v(t) = V_m e^{\sigma t} \cos(\omega t + \theta)$$

$$i(t) = I_m e^{\sigma t} \cos(\omega t + \phi)$$

$$s = \sigma + j\omega$$

$$v(t) = V_m e^{\sigma t} \cos(\omega t + \theta)$$

$$= \text{Re}(V_m e^{j\theta} e^{st})$$

Taking the real part of $v(t)/i(t)$
See notes in Part 3 A and B.

$$= \text{Re}(V_m e^{st})$$

Inductor:

$$v(t) = L \frac{d(I_m e^{st})}{dt} = sL I_m e^{st}$$

$$\text{Re}(V_m e^{st}) = sL I_m e^{st}$$

$$V_m e^{st} = sL I_m e^{st}$$

$$V_m = sL I_m$$

$$V = sL \cdot I$$

$$V(s) = sL \cdot I(s) \quad \text{<----}$$

$$s = \sigma + j\omega$$

$$i(t) = I_m e^{\sigma t} \cos(\omega t + \phi)$$

$$= \text{Re}(I_m e^{j\theta} e^{st})$$

$$= \text{Re}(I_m e^{st})$$

Capacitor:

$$v(t) = \frac{1}{C} \int I_m e^{st} dt = \frac{1}{sC} I_m e^{st}$$


$$\text{Re}(V_m e^{st}) = \frac{1}{sC} I_m e^{st}$$


$$V_m e^{st} = \frac{1}{sC} I_m e^{st}$$

$$V_m = \frac{1}{sC} I_m$$

$$V = \frac{1}{sC} I$$
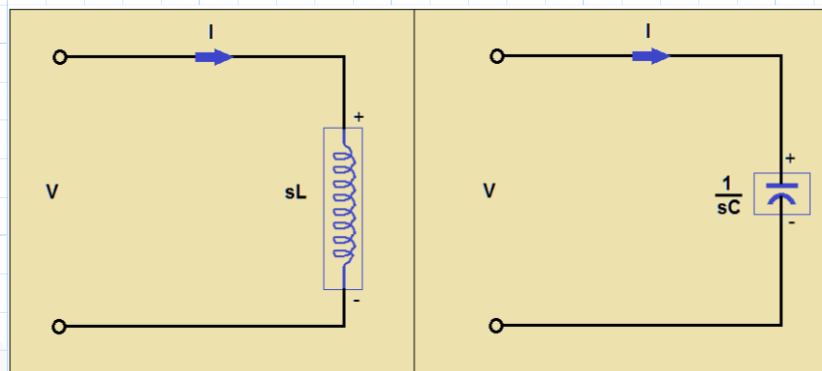
$$V(s) = \frac{1}{sC} I(s) \quad \text{<----}$$



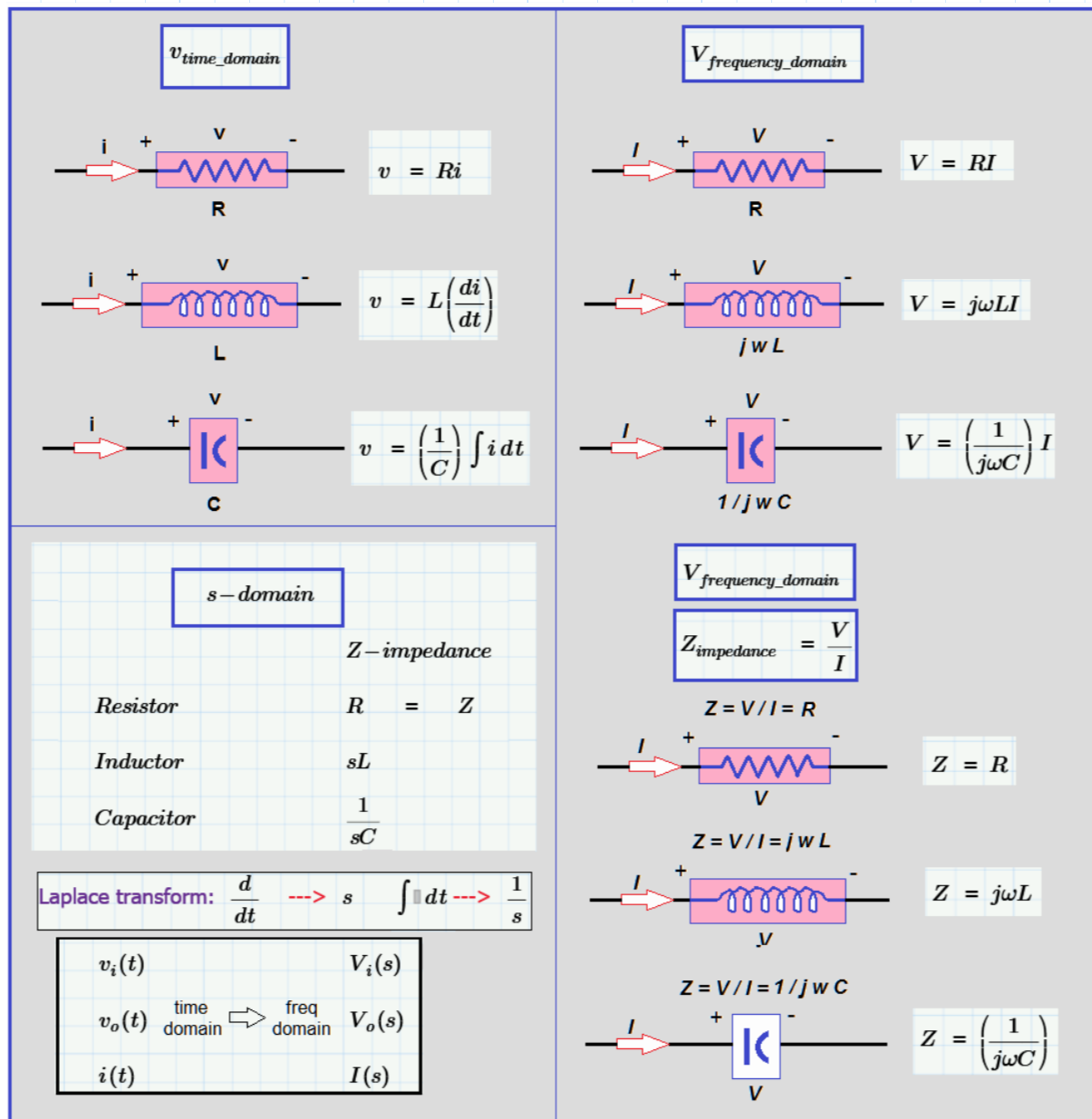


Derivative and Integral substitutes for s and $1/s$ for the component L and C respectively.

<p>Inductor: $v_L(t) = L \cdot \frac{di}{dt}$</p> <p>$\rightarrow V_L(s) = Ls \cdot I(s)$</p>	<p>Capacitor: $v_C(t) = \frac{1}{C} \int i dt$</p> <p>$\rightarrow V_C(s) = \frac{1}{sC} \cdot I(s)$</p>
---	--

Non-Commercial Use Only

Chp 1 Problem 1-1:

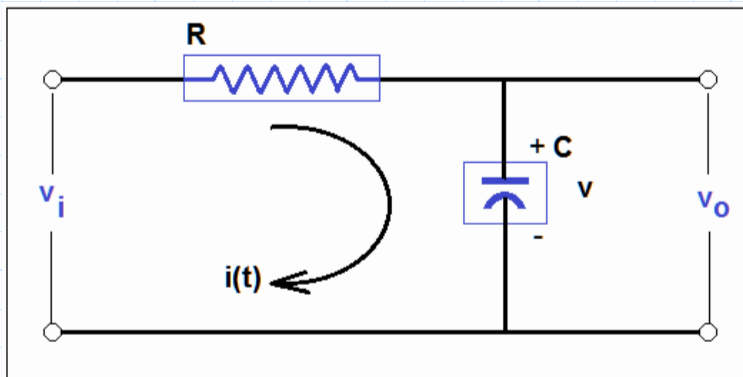

Derive the transfer function of the circuit shown in figure to the left.

Solution:

First thing is its a series circuit. We do a voltage conservation. Meaning the sum of voltages add to zero. You call that Kickoff's OR Kickout's Law.

The output is across the capacitor terminals.
The input is supply voltage for the resistor and capacitor.

$$v_i(t) = R \cdot i(t) + v_C(t) \quad i(t) \text{ is the circuit's current.}$$

$$\text{Set } v_o(t) = v_C(t) = \frac{1}{C} \int i \, dt$$

$$v_i(t) = R \cdot i(t) + v_o(t)$$

Now we convert the expression above to the s-domain.
Which in control systems textbook they say 'Taking the Laplace transform'.
Laplace Transforms starts with transfer functions in the s-plane or in terms of complex frequency. So, thats why we used a Controls textbook. Same.

$$V_i(s) = R I(s) + V_o(s)$$

$V_o(s)$ is that voltage across the capacitor C terminals, which we can set this in the s-domain of the capacitor.

$$V_o(s) = \frac{1}{sC} \cdot I(s) \quad \text{<--- C: } 1/sC, \text{ and } i(t): I(s).$$

Its more than forming a loop equation, we want to all the required variables in the expression so we can form that $V_o(s)/V_i(s)$.

How do we know what all terms and their forms we need before we can get to forming a transfer function?

Keep working in more and more example problems, partially looks like a guess, but after a few examples we get the general idea.

The Electrical Engineering expressions for defining components are formed in such a way that they have a future in advanced math where they can be manipulated in various ways to take full benefit of the math resulting in some output that serves a circuit's purpose - Karl Bogha.

$$V_o(s) = \frac{1}{sC} \cdot I(s)$$

$$I(s) = V_o(s) \cdot sC$$

$$V_i(s) = RI(s) + V_o(s) \quad <--- \text{ Lets plug in or if you prefer substitute the expression we got into this expression we formed earlier.}$$

$$\begin{aligned} V_i(s) &= R(V_o(s) \cdot sC) + V_o(s) \\ &= sRC(V_o(s)) + V_o(s) \end{aligned}$$


$$\begin{aligned} V_i(s) &= V_o(s) \cdot (sRC + 1) \quad <--- \text{ How would we had known that? Surely had to work examples.} \\ &= V_o(s) \cdot (1 + sRC) \quad \text{Keep clear of people and peers who say dont do the example go to the end of chapter problems, they lie so they have the edge - Engineer.} \end{aligned}$$

In the work place you never ever get problems to solve like hard end of chapter problems in hard core engineering textbooks, fake, it rarely help, most time you got all the time in the world - Karl Bogha.

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + sRC} \quad \text{Answer.}$$

Non-Commercial Use Only

Chp 1 Problem 1-2:

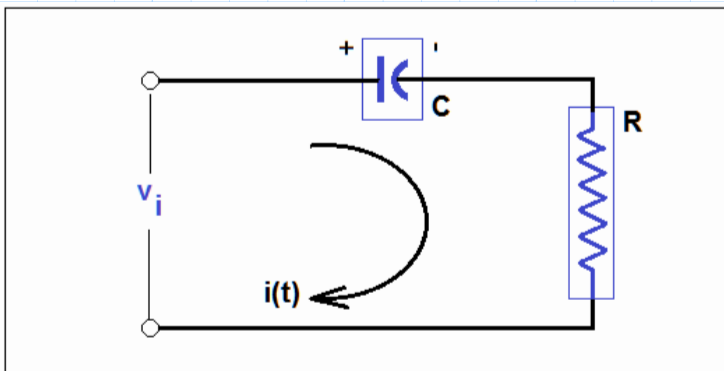

We seek the transfer function $I(s)/V_i(s)$?

Solution:

First thing is its a series circuit. We do a voltage conservation, meaning the sum of voltages add to zero. You call that *Kickoff's Law*!

$$v_i(t) = R \cdot i(t) + v_C(t) \quad i(t) \text{ is the circuit's current.}$$

$$v_C(t) = \frac{1}{C} \int i \, dt = \frac{1}{sC} I(s)$$

$$v_i(t) = R \cdot i(t) + v_C(t)$$

$$V_i(s) = RI(s) + \frac{1}{sC} I(s)$$

$$= RI(s) + \frac{1}{sC} I(s)$$

$$= I(s) \left(R + \frac{1}{sC} \right)$$


$$\frac{I(s)}{V_i(s)} = \frac{1}{\left(R + \frac{1}{sC} \right)} \quad \text{Simplify this term, multiply by } sC/R.$$

$$\frac{I(s)}{V_i(s)} = \frac{\left(\frac{sC}{R} \right)}{\frac{sC}{R} \left(R + \frac{1}{sC} \right)} = \frac{\left(\frac{sC}{R} \right)}{sC + \frac{1}{R}} = \left(\frac{1}{sC + \frac{1}{R}} \right) \frac{sC}{R} = \left(\frac{sC}{sCR + 1} \right)$$

$$\frac{I(s)}{V_i(s)} = \left(\frac{sC}{1 + sCR} \right) \quad \text{Answer.}$$

Good if we can work the final form of expression like this instead of the one a few steps before. It takes some extra effort to get it in a neat form that is more electric circuit friendly and meaningful.

Chp 1 Problem 1-3:

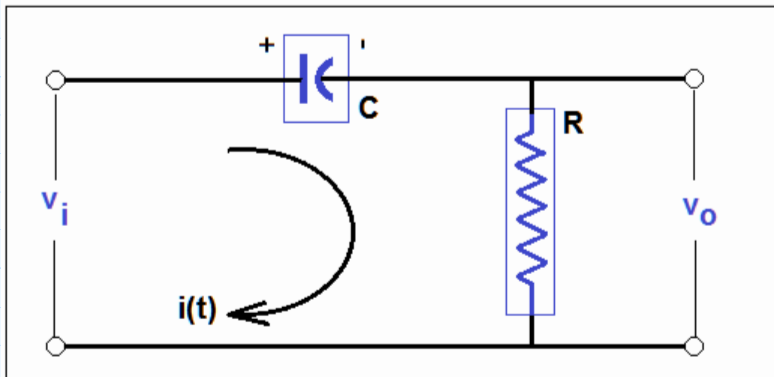

We seek the transfer function $V_o(s)/V_i(s)$?

Solution:

Conservation of voltage means something else?

I am not sure, when conserved it would remain the same.

So the sum equal zero in a loop. That for me is conserved.

Maybe they used it for something else. Usual I am not the first.

We kickoff with the voltage conservation.

$$V_i(t) = Ri(t) + \frac{1}{C} \int i(t) dt$$

$$\frac{1}{C} \int i(t) dt = \frac{1}{sC} \cdot I(s)$$

$$V_i(s) = RI(s) + \frac{I(s)}{sC}$$

Our circuit identifies voltage across resistor terminals as $V_o(t)$ which now becomes? $V_o(s)$ for the frequency domain.

$$V_o(s) = RI(s)$$

$$I(s) = \frac{V_o(s)}{R} \quad \text{Substitute in here:} \quad V_i(s) = RI(s) + \frac{I(s)}{sC}$$

$$V_i(s) = R \left(\frac{V_o(s)}{R} \right) + \left(\frac{V_o(s)}{R} \right) \cdot \frac{1}{sC} \quad \text{Isolate } V_o(s)$$

$$V_i(s) = V_o(s) \cdot \left(1 + \frac{1}{sCR} \right)$$

Next for the required transfer function:


$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\left(1 + \frac{1}{sCR}\right)} \quad \leftarrow \text{This can be simplified.}$$

Its awkward, that is why we simplify these awkward terms.

Multiply by sCR :

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\left(1 + \frac{1}{sCR}\right)} \cdot \frac{sCR}{sCR} = \frac{sCR}{(sCR + 1)} \quad \text{Answer.}$$

Chp 1 Problem 1-4:

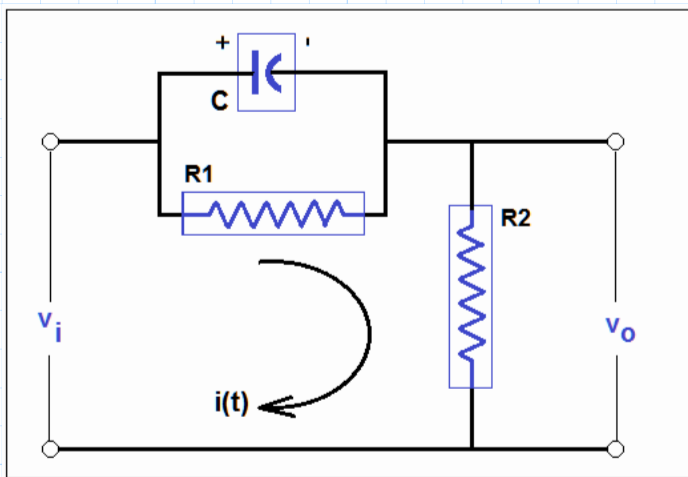

We seek the transfer function, $V_o(s)/V_i(s)$, of the electrical network shown to the left in phase lead form ?

Solution:

Z_1 is the parallel of C and R_1 :

$$\frac{1}{Z_1} = \frac{1}{R_1} + \frac{1}{\frac{1}{j\omega C}} = \frac{1}{R_1} + \frac{1}{\frac{1}{sC}} \quad \begin{matrix} s = \sigma + j\omega \\ \sigma = 0 \\ s = j\omega \end{matrix} \quad \begin{matrix} \text{We are concerned with} \\ \text{frequency, so we can set} \\ \text{sigma} = 0. \end{matrix}$$

$$\frac{1}{Z_1} = \frac{1}{R_1} + sC = \frac{1}{R_1} + \frac{sC}{1} \quad \text{multiply by } R_1$$


$$\frac{1}{Z_1} = \frac{R_1}{R_1} + \frac{sCR_1}{1} = \frac{R_1 + sCR_1}{1 \cdot R_1} = \frac{R_1 + sCR_1}{R_1}$$

$$\frac{1}{Z_1} = \frac{R_1}{R_1} + \frac{sCR_1}{R_1} = 1 + \frac{sCR_1}{R_1} = \frac{1 + sCR_1}{R_1}$$

Non-Commercial Use Only

Chapter 6 Part C. Solving Problems (Examples and Exercises). Source of study material: 1). Electric Circuits 6th Ed Schaums - Nahvi & Edminister. 2). Solutions & Problems of Control System - AK Jairath. 3). Engineering Circuits Analysis - Hyat & Kemmerly. My Homework. This is a pre-requisite study for Laplace Transforms in circuit analysis. Karl S. Bogha.
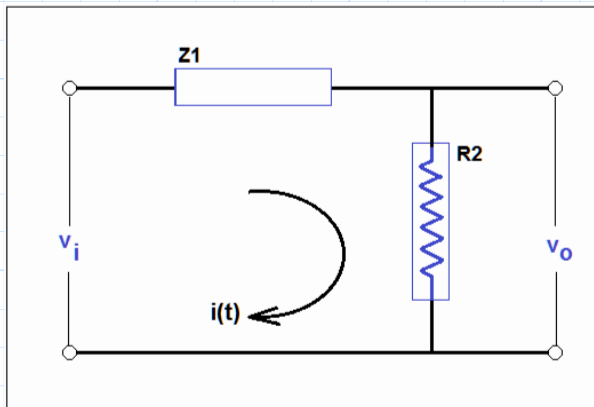
$$Z1 = \frac{R1}{1 + sCR1} \quad \text{After inverting.}$$



We kickoff with the voltage conservation.

$$v_i(t) = Z1I(s) + R2I(s)$$

$$v_o(t) = R2I(s)$$

Taking the Laplace Transform of the above 2 equation:

$$V_i(s) = Z1I(s) + R2I(s)$$

$$V_o(s) = R2I(s) \quad \text{Plug in equation above}$$

$$I(s) = \frac{V_o(s)}{R2} \quad \text{Plug in equation above}$$

$$V_i(s) = Z1\left(\frac{V_o(s)}{R2}\right) + V_o(s)$$

$$V_i(s) = V_o(s) \cdot \left(\frac{Z1}{R2} + 1\right) \quad \text{Plug in } Z1$$

$$V_i(s) = V_o(s) \cdot \left(\frac{\left(\frac{R1}{1 + sCR1}\right)}{R2} + 1\right)$$

$$= V_o(s) \cdot \left(\frac{\left(\frac{R1}{1 + sCR1}\right)}{R2} + \frac{R2}{R2}\right)$$

Non-Commercial Use Only

$$= V_o(s) \cdot \left(\frac{\left(\frac{R1}{1 + sCR1} \right) + R2}{R2} \right) \quad \text{Next rearrange and multiply by ---> } \frac{1 + sCR1}{1 + sCR1}$$

$$= \frac{V_o(s)}{R2} \cdot \left(\left(\frac{R1}{1 + sCR1} \right) + \frac{R2 \cdot (1 + sCR1)}{(1 + sCR1)} \right)$$

$$= \frac{V_o(s)}{R2} \cdot \left(\frac{R1 + R2 + sCR1R2}{1 + sCR1} \right)$$

$$= V_o(s) \left(\frac{R1 + R2}{R2} \right) \left(\frac{1 + sCR1R2}{1 + sCR1} \right) \quad \text{...not finished yet in this expression.}$$

$$V_i(s) = V_o(s) \left(\frac{R1 + R2}{R2} \right) \left(\frac{1 + \frac{sCR1R2}{R1 + R2}}{1 + sCR1} \right) \quad \text{Place } \frac{1}{R1 + R2} \text{ in there so it cancels the middle term } (R1 + R2)/R2 \text{ when multiplied.}$$

$$\frac{V_i(s)}{V_o(s)} = \left(\frac{R1 + R2}{R2} \right) \left(\frac{1 + \frac{sCR1R2}{R1 + R2}}{1 + sCR1} \right) \quad \text{Next invert both sides.}$$

$$\frac{V_o(s)}{V_i(s)} = \left(\frac{R2}{R1 + R2} \right) \left(\frac{1 + sCR1}{1 + \frac{sCR1R2}{R1 + R2}} \right) \quad \text{As provided in textbook.}$$

$$\frac{V_o(s)}{V_i(s)} = \left(\frac{R2}{R1 + R2} \right) \left(\frac{1 + sCR1}{1 + \left(\frac{R2}{R1 + R2} \right) sCR1} \right) \quad \text{Transfer function.}$$

We can simplify a little. Make RC the time constant in a series circuit = tau, and make the constant $R2/(R1 + R2) = a$. OR just any constant T.

$$T = CR1$$

$$a = \frac{R2}{R1 + R2}$$

$$\frac{V_o(s)}{V_i(s)} = a \left(\frac{1 + sT}{1 + asT} \right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{a \cdot (1 + sT)}{(1 + asT) T}$$

Answer.

Comment: Previous example problems used T for RC in the final transfer functions.

I left it out because my aim was the approach on how to get the transfer functions. T is not necessarily a time constant for this circuit.

You can verify. We could use P of Q but since its RLC, T or tau makes more sense.

Took time with the algebra otherwise a good easy example for most.

Chap 1 Problem 1.7 :

I jump to problem 1.7 because its the same circuit. This provides a continuity and not having to return later after several problems.

Derive the transfer function of the circuit shown (same circuit of problem 1.4).

If $v_i(t) = 8 \sin(10t)$ V, $R_1 = 50$ k Ohms, $R_2 = 5$ k Ohms and $C = 1$ uF.

Calculate the output voltage in magnitude and phase angle relative to input voltage?

Solution:

$$\text{Gain } G(s) = \frac{V_o(s)}{V_i(s)} = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{1 + sCR_1}{1 + \left(\frac{R_2}{R_1 + R_2} \right) sCR_1} \right)$$

$$\begin{aligned} k &:= 10^3 & M &:= 10^6 & u &:= 10^{-6} \\ R_1 &:= 50 \text{ k} & R_2 &:= 5 \text{ k} & C &:= 1 \text{ u} \end{aligned}$$

Substitute into transfer function:

$$\begin{aligned} G(s) &= \frac{V_o(s)}{V_i(s)} = R_2 \cdot \frac{(1 + sCR_1)}{(R_1 + R_2) + (sCR_1R_2)} \\ &= 5000 \left(\frac{1 + 0.05 s}{55000 + 250 s} \right) \quad \text{Divide numerator and denominator by 55,000.} \\ &= 0.091 \left(\frac{1 + 0.05 s}{1 + 0.0045 s} \right) \\ G(s) &= 0.01 \frac{(1 + 0.05 s)}{(1 + 0.0045 s)} \quad \text{Constant 0.091 rounded off to 0.01} \end{aligned}$$

$$\text{Zero: } (1 + 0.05 s)$$

$$\text{Pole: } (1 + 0.0045 s)$$

We are interested in $s = 0 + j\omega$, where $\sigma = 0$.

Hence we can analyse the frequency response.

Substitute s for $j\omega$ in transfer function.

Now we have $1 + 0.05s$ and $1 + 0.0045s$, this gives us the magnitude and angle for both. Since we have a real and imaginary part.

$$\begin{aligned} s &= \sigma + j\omega \\ \sigma &= 0 \\ s &= 0 + j\omega = j\omega \end{aligned}$$

$$G(j\omega) = 0.01 \frac{(1 + 0.05 j\omega)}{(1 + 0.0045 j\omega)}$$

Before we can calculate the angles we need the value of ω ?

$$v(t) = 8 \sin(10 \cdot t) \rightarrow A \sin(\omega t)$$

$$\omega = 10$$

$$\text{Zero: } (1 + 0.05 j 10) = 1 + 0.5j$$

$$\text{Pole: } (1 + 0.0045 j 10) = 1 + 0.045j$$

$$Z_Ang_G_s := \text{atan}\left(\frac{0.5}{1}\right) = 26.5651 \text{ deg}$$

$$P_Ang_G_s := \text{atan}\left(\frac{0.045}{1}\right) = 2.5766 \text{ deg}$$

$$Ang_G(s) = 26.565 - 2.577 = 23.988 \text{ degrees. Answer.}$$

Now for the magnitude of the transfer function, here is where the constant 0.1 is applied.

$$\text{Magnitude of zero: } \sqrt{1^2 + 0.5^2} = 1.118$$

$$\text{Magnitude of pole: } \sqrt{1^2 + 0.045^2} = 1.001$$

$$\text{Magnitude of } G(s): (0.1) \cdot \left(\frac{1.118}{1.001}\right) = 0.1117$$

The input signal is $v_i(t) = 8 \sin(\omega t)$

From which we can obtain the amplitude is 8 V maximum.

We next multiply the magnitude of $G(s)$ to 8V for the maximum output voltage.

$$\text{Amplitude} := 8.0 \quad \text{Mag}_G(s) := 0.1117$$

$$V_o := \text{Amplitude} \cdot \text{Mag}_G(s) = 0.894 \text{ V. Answer.}$$

Good example. Can be found in most circuits and all controls textbook.

Non-Commercial Use Only

Chap 1 Problem 1.8 :

Problem 1.8 is next here because it works on the same transfer function of problem 1.4. This is indicated in the problem statement, exact same circuit.

If $C = 1\mu\text{F}$ in the circuit of problem 1.4.

What values of R_1 and R_2 will give $T = 0.6$ sec, and $a = 0.1$

Solution:

$$G(s) = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{1 + sCR_1}{1 + \left(\frac{R_2}{R_1 + R_2} \right) sCR_1} \right) \quad T = CR_1 \quad a = \frac{R_2}{R_1 + R_2}$$

$$G(s) = \frac{a \cdot (1 + sT)}{(1 + asT)} \quad C := 1 \mu\text{F} \quad T := 0.6 \quad a := 0.1$$

$$CR_1 = 0.6, \text{ solve for } R_1: \quad CR_1 = 0.6$$

$$(1 \mu\text{F}) R_1 = 0.6$$

$$R_1 = \frac{0.6}{1 \cdot \mu} = 6 \cdot 10^5 \text{ Ohm.} = 0.6 \cdot \text{M Ohm. Answer.}$$

$$a = \frac{R_2}{R_1 + R_2} \quad \text{--->} \quad 0.1 = \frac{R_2}{600000 + R_2} \quad \text{--->} \quad 0.1 (600000 + R_2) = R_2$$


$$60000 + 0.1 R_2 = R_2$$

$$0.9 R_2 = 60000$$

$$R_2 = \frac{60000}{0.9} = 66666.7 = 0.066 \text{ M Ohms. Answer.}$$

Non-Commercial Use Only

Chp 1 Problem 1-5:

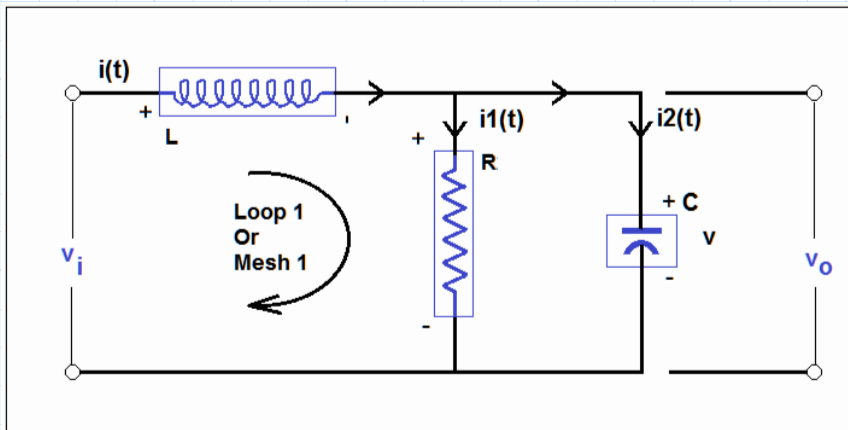

We seek the transfer function, $V_o(s)/V_i(s)$, of the electrical network shown to the left in phase lead form ?

Solution:

$$\text{Current at node: } i(t) = i_1(t) + i_2(t)$$

Voltage conservation in loop at left side:

$$v_i(t) = L \frac{di}{dt} + Ri_1(t)$$

Next, in a clever way, we pull in the $v_o(t)$ relationship thru the capacitor voltage, where C is voltage across resistor R , and we know $v_o(t)$ is the voltage across the capacitor.

$$v_o(t) = Ri_1(t) = \frac{1}{C} \int i_2(t) dt$$

$$v_i(t) = L \frac{di}{dt} + Ri_1(t)$$

$$V_i(s) = sLI(s) + RI_1(s)$$

$$RI_1(s) = \frac{1}{C} \int i_2(t) dt = \frac{1}{sC} I_2(s)$$

$$RI_1(s) = V_o(s) = \frac{I_2(s)}{sC}$$

Non-Commercial Use Only

$$\text{Voltage across R: } V_o(s) = \frac{I_2(s)}{sC} = RI_1(s) \text{ thus } I_1(s) = \frac{V_o(s)}{R}$$

$$\text{We update our } I(s) \text{ expression here } V_i(s) = sLI(s) + RI_1(s)$$

$$i(t) = i_1(t) + i_2(t)$$

$$I(s) = I_1(s) + I_2(s)$$

$$V_i(s) = sL(I_1(s) + I_2(s)) + RI_1(s)$$

$$V_i(s) = sL(I_1(s) + I_2(s)) + V_o(s)$$

$$\text{Substitute voltage across C for R: } V_o(s) = \frac{I_2(s)}{sC}$$

$$sCV_o(s) = I_2(s)$$

$$V_i(s) = sL\left(\frac{V_o(s)}{R} + sCV_o(s)\right) + V_o(s)$$

$$V_i(s) = V_o(s) + sL\left(\frac{V_o(s)}{R} + sCV_o(s)\right)$$

$$V_i(s) = V_o(s) + V_o(s) \cdot \left(\frac{sL}{R} + sCsL\right)$$

$$V_i(s) = V_o(s) \cdot \left(1 + \frac{sL}{R} + s^2 LC\right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\left(1 + \frac{sL}{R} + s^2 LC\right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\left(s^2 LC + \frac{sL}{R} + 1\right)}$$

Answer. Lots of substitutions.
A compact answer below.

The Engineer makes the expression simpler in appearance, quadratic expression, thru the use of variable T1 and T2. T1 = L/R maybe a time constant but not here. T2 = CR which is NOT a time constant, you verify should it be of concern.


Chapter 6 Part C. Solving Problems (Examples and Exercises). Source of study material: 1). Electric Circuits 6th Ed Schaums - Nahvi & Edminister. 2). Solutions & Problems of Control System - AK Jairath. 3). Engineering Circuits Analysis - Hyat & Kemmerly. My Homework. This is a pre-requisite study for Laplace Transforms in circuit analysis. Karl S. Bogha.

$$T1 = \frac{L}{R} \quad T2 = CR$$

$$T1T2 = \left(\frac{L}{R}\right)(CR) = LC$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{(T1T2s^2 + T1s + 1)} \quad \text{Answer.}$$

Chp 1 Problem 1-6:

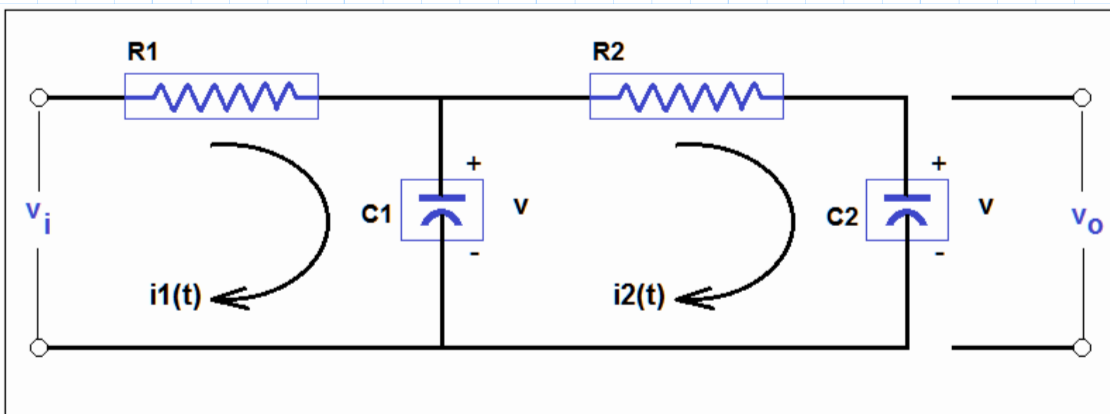

We seek the transfer function, $V_o(s)/V_i(s)$, of the electrical network shown above ?

Solution:


Set up the impedance Z for each component:

$$Z1 = R1$$

$$Z2 = \frac{1}{sC1}$$

$$Z3 = R2$$

$$Z4 = \frac{1}{sC2}$$

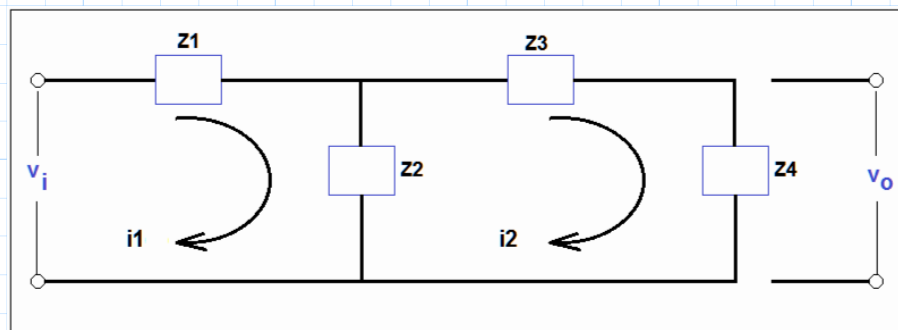

Non-Commercial Use Only

Voltage mesh/loop equations in Laplace:

Left loop:

$$V_i(s) = Z_1 I_1(s) + Z_2 (I_1 - I_2)$$

$$V_i(s) = I_1(s) (Z_1 + Z_2) - Z_2 I_2 \quad \dots \text{Eq 1}$$

Right loop:

$$0 = Z_2 (I_2 - I_1) + Z_3 I_2(s) + Z_4 I_2(s)$$

$$0 = -Z_2 I_1 + I_2(s) (Z_2 + Z_3 + Z_4) \quad \dots \text{Eq 2}$$

Next we form an expression for V_o :

$$V_o(s) = Z_4 I_2(s) \quad \dots \text{Eq 3}$$

If I am correct, from these few examples we seen, we want to place one expression for current, into the the other equation, then work towards the transfer function, provided we have $V_o(s)$ and $V_i(s)$ in that expression to work with.

Here, $I_1(s)$ looks the better simpler choice to place in Eq 2.

Because we do not have a voltage source on the RHS.

Then we set $V_o(s)$ for $Z_4 I_2(s)$.

Then work with the equation which can fit-in V_o , V_i , and I_1 and I_2 in it.

If we dont have it yet continue re-hashing.

What you think, that's the plan? *Of course!*

$$0 = -Z_2 I_1 + I_2(s) (Z_2 + Z_3 + Z_4) \quad \dots \text{Eq 2}$$

$$I_1(s) Z_2 = I_2(s) (Z_2 + Z_3 + Z_4)$$

$$I_1(s) = \frac{I_2(s) (Z_2 + Z_3 + Z_4)}{Z_2}$$

$$V_i(s) = I_1(s) (Z_1 + Z_2) - Z_2 I_2 \quad \dots \text{Eq 1, substitute } I_1(s)$$

$$V_i(s) = \frac{I_2(s) (Z_2 + Z_3 + Z_4) \cdot (Z_1 + Z_2)}{Z_2} - Z_2 I_2(s) \quad \text{Fix for } Z_2 \text{ at very right of numerator.}$$

$$V_i(s) = \frac{I_2(s) \cdot ((Z_2 + Z_3 + Z_4) \cdot (Z_1 + Z_2))}{Z_2} - \frac{Z_2 Z_2 I_2(s)}{Z_2}$$

$$V_i(s) = \frac{I_2(s) \cdot ((Z_2 + Z_3 + Z_4) \cdot (Z_1 + Z_2) - Z_2^2)}{Z_2}$$

$$\frac{V_i(s)}{I_2(s)} = \frac{((Z_2 + Z_3 + Z_4) \cdot (Z_1 + Z_2) - Z_2^2)}{Z_2}$$

For me this is new, not a twist but certainly new I don't remember doing a substitution on the LHS! Ok Not typical. Hope I am gaining skills here.

$$V_o(s) = Z_4 I_2(s) \quad \dots \text{Eq 3}$$

$$I_2(s) = \frac{V_o(s)}{Z_4}$$

Substitute this in the expression $V_i(s)/I_2(s)$

$$\frac{V_i(s)}{\left(\frac{V_o(s)}{Z_4}\right)} = \frac{((Z_2 + Z_3 + Z_4) \cdot (Z_1 + Z_2) - Z_2^2)}{Z_2}$$

$$\frac{V_i(s)}{V_o(s)} = \frac{((Z_1 + Z_2) \cdot (Z_2 + Z_3 + Z_4) - Z_2^2)}{Z_2 \cdot Z_4}$$

Invert the expression so we get $V_o(s)$ in the numerator.

$$\frac{V_o(s)}{V_i(s)} = \frac{Z_2 \cdot Z_4}{((Z_1 + Z_2) \cdot (Z_2 + Z_3 + Z_4) - Z_2^2)}$$

Lets expand the denominator expression:

$$(Z_1 + Z_2) \cdot (Z_2 + Z_3 + Z_4) = Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_2 + Z_2 Z_3 + Z_2 Z_4$$

Now for the full denominator expression:

$$= Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_2 + Z_2 Z_3 + Z_2 Z_4 - Z_2 Z_2$$

$$= Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4$$

$$\frac{V_o(s)}{V_i(s)} = \frac{Z_2 \cdot Z_4}{Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4} \quad \text{The transfer function.}$$

Next we substitute the values of impedances $Z1...Z4$:

$$\frac{V_o(s)}{V_i(s)} = \frac{Z2 \cdot Z4}{Z1Z2 + Z1Z3 + Z1Z4 + Z2Z3 + Z2Z4}$$

$$Z1 = R1 \quad Z2 = \frac{1}{sC1} \quad Z3 = R2 \quad Z4 = \frac{1}{sC2}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC1} \cdot \frac{1}{sC2}}{\frac{R1}{sC1} + R1R2 + \frac{R1}{sC2} + \frac{R2}{sC1} + \frac{1}{s^2 C1C2}}$$

As usual these types expressions are made simpler, especially in electric circuits. It helps in building the physical circuit. Which I almost forgot the true purpose here. We are building circuits and components are to be put together on a bread board for testing. Hello?...true purpose? Why not?

$$= \left(\frac{1}{\frac{R1}{sC1} + R1R2 + \frac{R1}{sC2} + \frac{R2}{sC1} + \frac{1}{s^2 C1C2}} \right) \cdot \frac{1}{sC1} \cdot \frac{1}{sC2}$$

$$= \frac{1}{R1sC2 + R1R2 \cdot s^2 C1C2 + R1sC1 + R2sC2 + 1}$$

Multiplied by $sC1 \ sC2$ top and bottom.

$$= \frac{1}{sR1C2 + s^2 R1R2 \cdot C1C2 + sR1C1 + sR2C2 + 1}$$

$$= \frac{1}{sR1C2 + sR1C1 + sR2C2 + 1 + s^2 R1R2 \cdot C1C2}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + s(R1C2 + R1C1 + R2C2) + s^2 R1R2 \cdot C1C2}$$

Answer.

The denominator is a neat 2nd order expression. The circuit is also a practical circuit for application in electric circuits, electronics and other electrical/electronic applications.

Non-Commercial Use Only

Chp 1 Problem 1.11:

Problem 1.11 comes here because this problem has a similar transfer function to problem 1.6. As indicated in the problem statement of 1.11. The changes being only in the arrangement of components, that being the swap between R and C.


Determine the transfer function relation $V_o(s)$ to $V_i(s)$ for the circuit.

Calculate output voltage $t > 0$ for a unit step voltage input at $t = 0$.

Solution:

In 1.6 we used the impedance Z to construct the transfer function. Later we plugged in the values for Z 's. So that's why this transfer function is relevant.
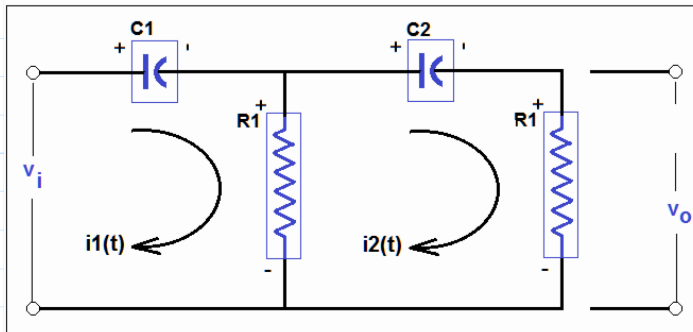
$$\frac{V_o(s)}{V_i(s)} = \frac{Z_2 \cdot Z_4}{Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4} \quad \leftarrow \text{From problem 1.6}$$




\leftarrow This is the circuit for problem 1.8.

$$u := 10^{-6} \quad M := 10^6$$

$$C1 := 1 \text{ u F} \quad C2 := 0.5 \text{ u F}$$

$$R1 := 1 \text{ M} \quad R2 := 1 \text{ M}$$

The Z impedance circuit becomes:

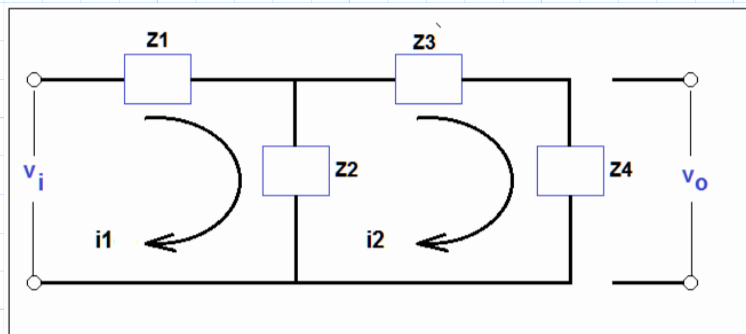

We make 10^6 the common multiplier for resistors and 10^{-6} for capacitor. Now we only need work with the simple numbers.

$$Z1 = \frac{1}{s} \quad Z2 = 1$$

$$Z3 = \frac{1}{0.5 s} \quad Z4 = 1$$

$$\frac{V_o(s)}{V_i(s)} = \frac{Z_2 \cdot Z_4}{Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4}$$

$$= \frac{1 \cdot 1}{\left(\frac{1}{s}\right) \cdot 1 + \left(\frac{1}{s}\right) \left(\frac{1}{0.5 s}\right) + \left(\frac{1}{s}\right) (1) + (1) \left(\frac{1}{0.5 s}\right) + (1) (1)}$$

$$\begin{aligned}
 &= \frac{1}{\frac{1}{s} + \left(\frac{1}{0.5 s^2}\right) + \left(\frac{1}{s}\right) + \left(\frac{1}{0.5 s}\right) + 1} \quad \text{Multiply by } s^2 \\
 &= \frac{s^2}{s + 2 + s + 2 s + s^2} = \frac{s^2}{2 + 4 s + s^2} = \frac{s^2}{s^2 + 4 s + 2} \\
 \frac{V_o(s)}{V_i(s)} &= \frac{s \cdot s}{s^2 + 4 s + 2}
 \end{aligned}$$

Unit step voltage comes on at $t=0$ and is of unit value, ie 1. $V_i(s)$ must equal 1.

$$V_o(s) = \frac{V_i(s) \cdot s \cdot s}{s^2 + 4 s + 2} = \frac{1 \cdot s \cdot s}{s^2 + 4 s + 2}$$

$$s_{z1} := 1 \quad V_o(s) = \frac{s}{s^2 + 4 s + 2}$$

$$ax^2 + bx + c : s^2 + 4 s + 2$$

$$s_1 = \frac{-b - \sqrt{b^2 - 4ac}}{2a} = \frac{-4 - \sqrt{4^2 - 4 \cdot 1 \cdot 2}}{2 \cdot 1} = -3.4142$$

$$s_2 = \frac{-b + \sqrt{b^2 - 4ac}}{2a} = \frac{-4 + \sqrt{4^2 - 4 \cdot 1 \cdot 2}}{2 \cdot 1} = -0.5858$$

We solved the denominator for the poles. Which math wise were the roots but electrical wise these are the poles.

$$V_o(s) = \frac{s^2}{(s + 3.414) \cdot (s + 0.586)} \quad \text{The poles going back in the transfer function with the opposite sign.$$

For the pole to be maximum s_1 and s_2 ? -3.414 and -0.586

What about the numerator what any value to solve?

Its NOT the numerator its the COEFFICIENTS of $V_o(s)$ and those same for time domain.

At $t < 0$ $V_o(<0) = 0$, and $t > 0$ $V_o(>0) = 0$, but for $t > 0$ $V_o(>>0) = 1u(t)$.

At -0 its near same as $0+$ equal 0. So we use continuity here?

No, basically math. To solve for coefficients using the?

Method of proper fractions OR Equating coefficients of like powers.

Next calculate the coefficients.

$$V_o(s) = \frac{s^2}{(s + 3.414) \cdot (s + 0.586)} \quad \text{Split LHS to solve for coefficients.}$$

$$\frac{s \cdot s}{(s + 3.414) \cdot (s + 0.586)} = \frac{A}{(s + 3.414)} + \frac{B}{(s + 0.586)} \quad \text{2nd order eq.}$$

$$A(s + 0.586) + B(s + 3.414) = As + 0.586A + Bs + B3.414$$

Arrange like terms: *s below is numerator term in transfer function - s*s split to s*s.
One 's' for 1 equation (As+Bs) = 1 <---coefficient of s = 1. Like terms.*

$$\begin{array}{rclcl} As + Bs & = & s & \text{--->} & A + B = 1 & \text{Eq 1} \\ 0.586A + 3.414B & = & 0 & \text{--->} & 0.586A + 3.414B = 0 & \text{Eq 2} \end{array}$$

$$\begin{array}{rclcl} 0.586A + 0.586B & = & 0.586 & \text{Eq 1} \times 0.586 \dots \text{Eq 3} \\ 0.586A + 3.414B & = & 0 & \text{Eq 2} \end{array}$$

$$\begin{array}{rclcl} (0.586 - 3.414)B & = & 0.586 & \text{Eq 3} - \text{Eq 2} \\ (0.586 - 3.414) & = & -2.828 & \\ -2.828B & = & 0.586 & \end{array}$$

$$B = \frac{0.586}{-2.828} = -0.2072$$

$$\begin{array}{rclcl} A + B & = & 1 \\ A - 0.207 & = & 1 \\ A & = & 1 + 0.207 = 1.207 \end{array}$$

The circuit s-domain: $V_o(s) = \frac{A}{(s + 3.414)} + \frac{B}{(s + 0.586)}$

$$V_o(s) = \frac{1.21}{(s + 3.414)} - \frac{0.21}{(s + 0.586)}$$


The general form of $v_o(t)$: $Ae^{-s1 \cdot t} + Be^{-s1 \cdot t}$

$$v_o(t) = 1.21 e^{-3.414 \cdot t} - 0.21 e^{-0.586 \cdot t} \quad \text{Answer.}$$

Interesting solution math wise. What math can do for determining coefficients by 'equating coefficients of like powers'.

Non-Commercial Use Only

Chp 1 Problem 1.9:

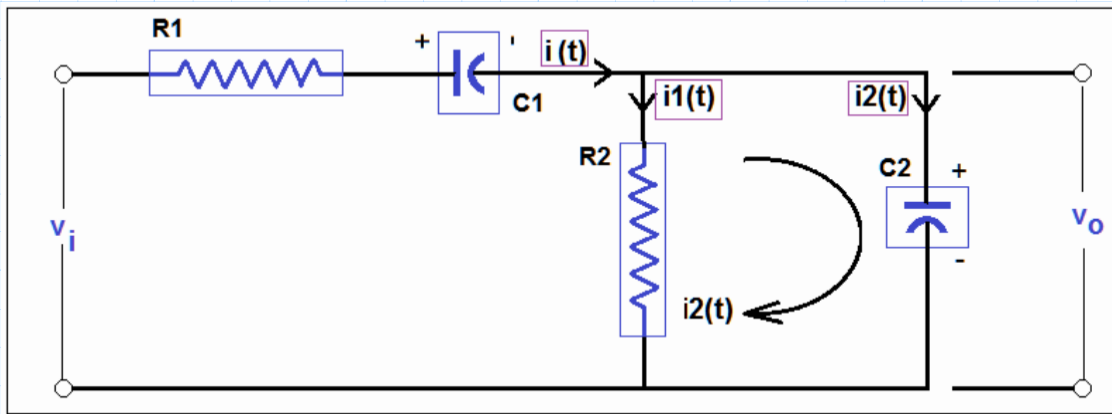

Find the transfer function of the network shown in figure above.
Plot its poles and zeros for $R1 = R2 = 1$, and $C1 = C2 = 1$.

Solution:

Current equation at node:

$$i(t) = i_1(t) + i_2(t) \quad \text{Note: Current thru } R1 \text{ and } C1 \text{ is } i(t).$$

Voltage mesh equations:

$$v_i(t) = R1 i(t) + \frac{1}{C1} \cdot \int i \, dt + R2 \cdot ((i_1(t) - i_2(t)))$$

Deviation here: $R2 \cdot ((i_1(t) - i_2(t)))$ we neglect $i_2(t)$ leaving $\rightarrow R2 i_2(t)$
Shown later.

Voltage across $R2$ is $V_o(t)$.

Form the voltage mesh equation using $V_o(t)$.

$$v_o(t) = R2 \cdot ((i_2(t) - i_1(t))) + \frac{1}{C2} \cdot \int i_2(t) \, dt \quad \text{We may not need this mesh equation.}$$

We did this just so we see the time domain equations, we could have started with to s-domain as we did in other example(s).

Now for converting to s-domain,
in other words taking the Laplace Transform:

$$I(s) = I_1(s) + I_2(s)$$

$$V_i(s) = R_1 I(s) + \frac{1}{sC_1} I(s) + R_2 \cdot (I_1(s) - I_2(s))$$

$$V_o(s) = R_2 \cdot (I_2(s) - I_1(s)) + \frac{1}{sC_2} \cdot I_2(s) \quad \text{We may not need this equation.}$$

The voltage across C2 is the same across R2.

This is the voltage $v_o(t)$ or $V_o(s)$.

We can use this voltage expression and plug into the $V_i(s)$ equation.

Obviously we want to plug in for $R_2 I_1(s)$.

$$v_o(t) = \frac{1}{C_2} \int i_2(t) dt$$

$$= R_2 \cdot i_1(t) \quad \text{Here we do not do a mesh method on the current thru R2. We simply identify it to } i_1(t), \text{ since its the voltage across the resistor terminals equated to } v_o(t).$$


Their Laplace transform:

$$V_o(s) = \frac{1}{sC_2} I_2(s)$$

$$= R_2 \cdot I_2(s)$$

$$V_i(s) = R_1 I(s) + \frac{1}{sC_1} I(s) + R_2 \cdot (I_1(s) - I_2(s)) \quad \text{The main equation now.}$$
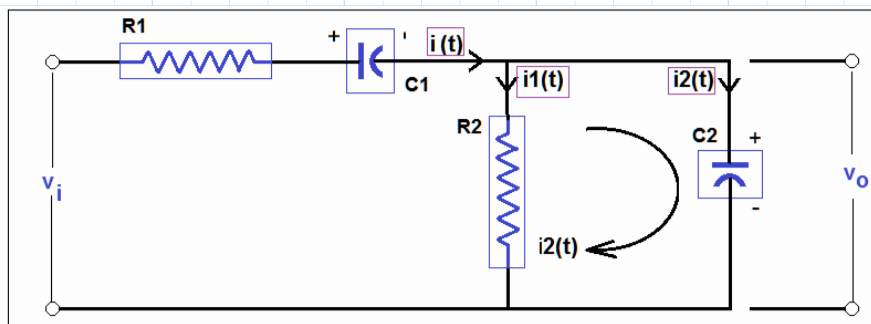
$$V_i(s) = R_1 I(s) + \frac{1}{sC_1} I(s) + R_2 \cdot I_1(s) - R_2 I_2(s) \quad \text{Plug in } V_o \text{ at } R_2 I_1(s)$$



$$V_i(s) = R_1 I(s) + \frac{1}{sC_1} I(s) + V_o(s) - R_2 I_2(s)$$

Mesh or voltage loop problem, stated earlier below.

Deviation here: $R_2 \cdot ((i_1(t) - i_2(t)))$ we neglect $i_2(t)$ leaving $\rightarrow R_2 i_1(t)$

Few attempts to find a substitute for $R2I2(s)$ was not obtained.

The equation, voltage conservation, by the author-engineer did not include the $i2(t)$ expression for $R2$. The engineer is taking $i1(t)$ as a known current or on its own. So there is no need for $R2(i1(t) - i2(t))$, rather just $R2i1(t)$.

The engineer's solution stated the assumption current distribution as shown below. I did it taking two loops, mesh equations, until I knew why. Otherwise the assumption would not been clear to me. Thus I leave it as it is, with correction continued below.

The improved or updated voltage equation becomes:

$$\begin{aligned} v_i(t) &= R1i(t) + \frac{1}{C1} \cdot \int i \, dt + R2 \cdot ((i1(t) - i2(t))) \\ v_i(t) &= R1i(t) + \frac{1}{C1} \cdot \int i \, dt + R2 \cdot i1(t) \\ V_i(s) &= R1I(s) + \frac{1}{sC1} I(s) + R2I1(s) \end{aligned}$$

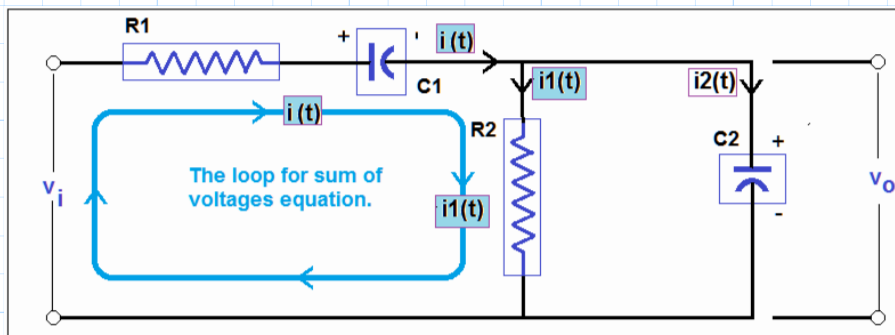


Figure to left is the voltage loop given $i1(t)$ and $i2(t)$ are known values.

$$V_o(t) = R2 \cdot I1(s) \quad \text{Plug in equation above.}$$

$$V_i(s) = R1I(s) + \frac{1}{sC1} I(s) + V_o(s)$$

$$I(s) = I1(s) + I2(s) \quad \text{Plug in equation below.}$$


$$V_i(s) = R1(I1(s) + I2(s)) + \frac{1}{sC1} (I1(s) + I2(s)) + V_o(s)$$

Rearranging:

$$V_i(s) = (I1(s) + I2(s)) \left(R1 + \frac{1}{sC1} \right) + V_o(s)$$

I cannot find a $V_o(s)/V_i(s)$ from the above expression.

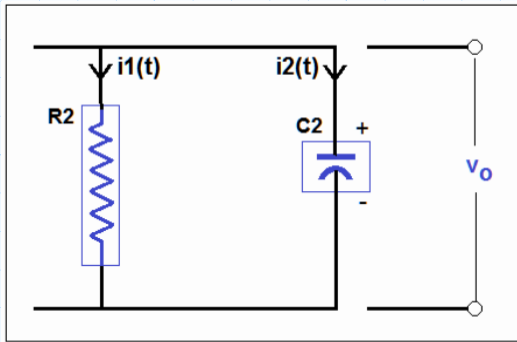Clever engineer does a substitution for $I1(s)$ and $I2(s)$.



$$V_o(s) = R1 I1(s)$$

$$I1(s) = \frac{V_o(s)}{R1}$$

$$V_o(s) = \frac{1}{sC2} I2(s)$$

$$I2(s) = sC2 V_o(s)$$

Substitute the expressions for $I1(s)$ and $I2(s)$ into the $V_i(s)$ equation.

$$V_i(s) = (I1(s) + I2(s)) \left(R1 + \frac{1}{sC1} \right) + V_o(s)$$

$$V_i(s) = \left(\frac{V_o(s)}{R1} + sC2 V_o(s) \right) \left(R1 + \frac{1}{sC1} \right) + V_o(s)$$

$$V_i(s) = V_o(s) \cdot \left(\frac{1}{R1} + sC2 \right) \left(R1 + \frac{1}{sC1} \right) + V_o(s)$$

Another new trick, maybe not, but not common divide by $V_o(s)$

$$\frac{V_i(s)}{V_o(s)} = \left(\frac{1}{R1} + sC2 \right) \left(R1 + \frac{1}{sC1} \right) + 1$$

Multiply the parenthesis: $\frac{R1}{R1} + \frac{1}{sC1R1} + sC2R1 + \frac{sC2}{sC1}$ Note: $C1 = C2$

$$= 1 + \frac{1}{sC1R1} + sC2R2 + 1$$

$$\frac{V_i(s)}{V_o(s)} = 1 + \frac{1}{sC1R1} + sC2R2 + 1 + 1$$

$$\frac{V_i(s)}{V_o(s)} = \frac{1}{sC1R1} + sC2R2 + 3$$

Invert for $V_o(s)/V_i(s)$: $\frac{V_o(s)}{V_i(s)} = \frac{1}{\frac{1}{sC1R1} + sC2R2 + 3}$

Next simplify this expression for the purpose of attaining an expression in s form.

The s form of expression we seek where we can identify zeros and poles.

$$\begin{aligned}\frac{V_o(s)}{V_i(s)} &= \frac{1}{\frac{1}{sC_1R_1} + sC_2R_2 + 3} \quad \text{Multiply top and bottom by } sC_1R_1 \\ &= \frac{sC_1R_1}{1 + (sC_1R_1)(sC_2R_2) + 3(sC_1R_1)} \\ &= \frac{sC_1R_1}{1 + (s^2 \cdot C_1C_2R_1R_2) + 3sC_1R_1}\end{aligned}$$

$$\begin{aligned}\text{Let } C &= C_1 = C_2 = 1 \\ R &= R_1 = R_2 = 1\end{aligned}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{sCR}{1 + (s^2 \cdot C^2 \cdot R^2) + 3sCR} \quad \begin{array}{l} \text{Since } R_1=R_2=C_1=C_2=1 \\ \text{We substitute for 1.} \end{array}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{s}{1 + s^2 + 3s} = \frac{s}{s^2 + 3s + 1} \quad \text{Answer for transfer function.}$$

Zero: 0 **Answer.**

Pole(s): Solve quadratic equation $s^2 + 3s + 1$

$$\begin{aligned}As^2 + Bs + C \quad s_1 \ s_2 &= \frac{-B \pm \sqrt{B^2 - 4AC}}{2A} \\ s_1 &= \frac{-3 + \sqrt{3^2 - (4 \cdot 1 \cdot 1)}}{2 \cdot 1} = -4 \cdot 10^{-1} \\ s_2 &= \frac{-3 - \sqrt{3^2 - (4 \cdot 1 \cdot 1)}}{2 \cdot 1} = -3\end{aligned}$$

Poles: -0.382 and -2.618 **Answer.**

The manual plot is easy, real x-axis and imaginary y-axis.
Here all the zero and poles are on the x-axis at 0, -0.382, and -2.618.

Lets try plotting the functions, numerator and denominator.

Non-Commercial Use Only

Chapter 6 Part C. Solving Problems (Examples and Exercises). Source of study material: 1). Electric Circuits 6th Ed Schaums - Nahvi & Edminister. 2). Solutions & Problems of Control System - AK Jairath. 3). Engineering Circuits Analysis - Hyat & Kemmerly. My Homework. This is a pre-requisite study for Laplace Transforms in circuit analysis. Karl S. Bogha.


Origin (1, 1)

Set start of matrix at 1,1.

$$Z := \begin{bmatrix} 0 & 0 \end{bmatrix}$$


$$P := \begin{bmatrix} -0.382 & 0 \\ -2.618 & 0 \end{bmatrix}$$

Using matrix Z for zero and P for poles.

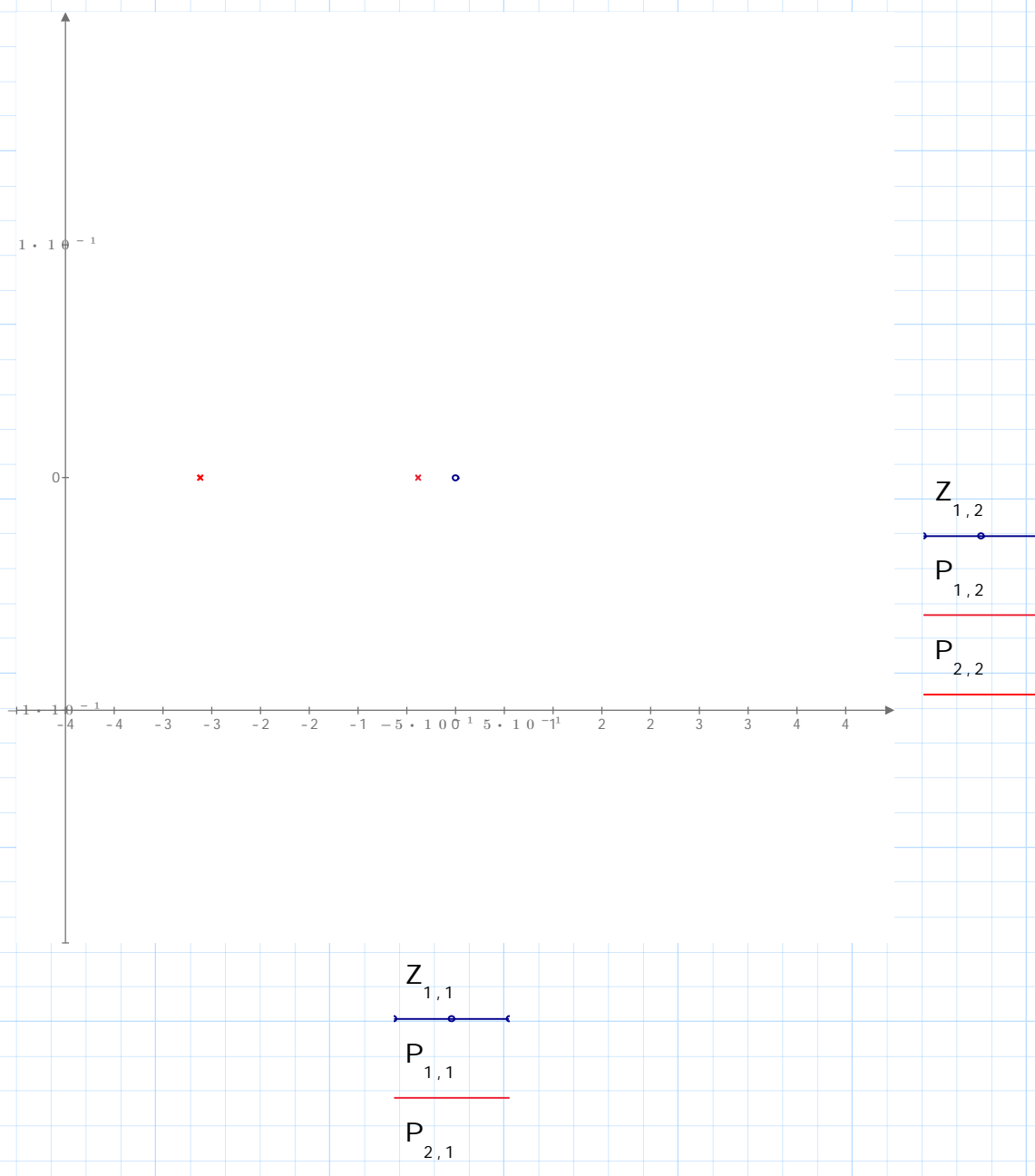

Answer. Plot above.

Chp 1 Problem 1.10:

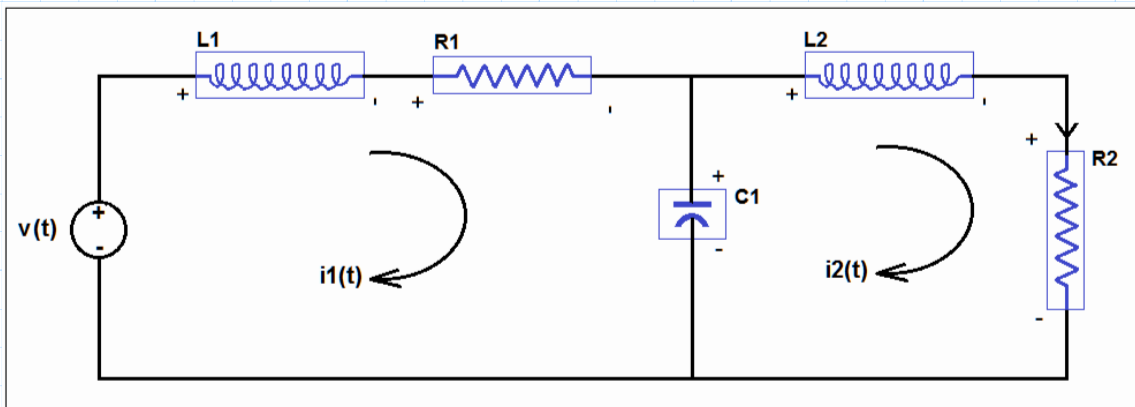

Write the differential equations for the electrical circuit above.

Solution:

I kickoff with the sum of voltage around a loop equal zero.
I do an equation for each loop.

Loop $i_1(t)$:

$$v_i(t) = L_1 \left(\frac{di_1(t)}{dt} \right) + R_1 i_1(t) + \frac{1}{C_1} \cdot \int i_1(t) dt - \frac{1}{C_1} \cdot \int i_2(t) dt$$

Loop $i_2(t)$:

$$0 = L_2 \left(\frac{di_2(t)}{dt} \right) + R_2 i_2(t) + \frac{1}{C_1} \cdot \int i_2(t) dt - \frac{1}{C_1} \cdot \int i_1(t) dt$$

Answer.


Not part of the question but how if I did a s-domain on the time domain, what the typical controls engineering course will say is taking the Laplace transform? You verify.

$$V_i(s) = sL_1 \cdot I_1(s) + R_1 \cdot I_1(s) + \frac{1}{sC_1} \cdot I_1(s) - \frac{1}{sC_1} \cdot I_2(s)$$

$$0 = sL_2 \cdot I_2(s) + R_2 \cdot I_2(s) + \frac{1}{sC_1} \cdot I_2(s) - \frac{1}{sC_1} \cdot I_1(s) \quad \text{Answer.}$$

Non-Commercial Use Only


Chp 1 Problem 1.12:

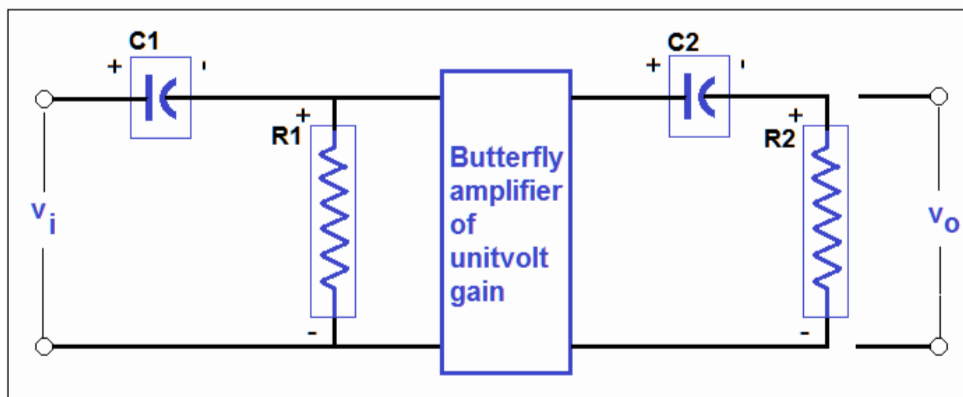

Determine the transfer function relating $V_o(s)$ to $V_i(s)$ for network above. Calculate the output voltage, $t > 0$, for a unit step voltage input at $t=0$, when $C1 = 1 \mu F$, $R = 1 \text{ M Ohm}$, $C2 = 0.5 \mu F$ and $R2 = 1 \text{ M Ohm}$.

Solution:

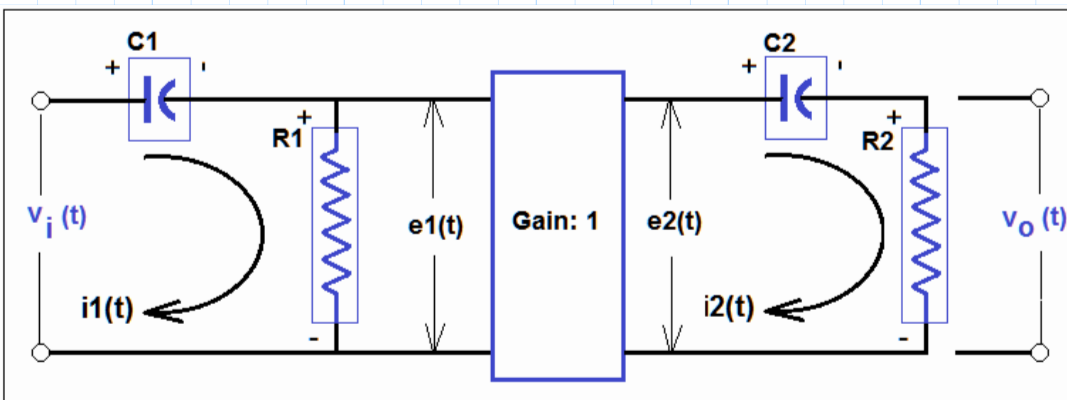Circuit re-sketched for applying sum of voltage in a loop method. Kickoff's Voltage Law, KVL, usually what the electrical engineer calls.



Amplifier gain $e2(t)/e1(t) = 1$. Therefore $e1(t) = e2(t)$. The circuit has a voltage input $v_i(t)$, and to the output side of the amplifier is a voltage gained $e2(t)$ this is similar to supplying voltage to the circuit to the right of the amplifier.

We proceed with KVL on the left and right, and we equate the resistor $R1$ voltage for $e1(t)$.

$$v_i(t) = \frac{1}{C1} \int i1(t) dt + R1i1(t)$$

$$e2(t) = \frac{1}{C2} \int i2(t) dt + R2i2(t)$$

$$e1(t) = R1i1(t) \quad \text{Amplifier left side voltage.}$$

$$v_o(t) = R2i2(t) \quad \text{Amplifier right side voltage.}$$

This being the voltage output $v_o(t)$

Now we take the Laplace transforms of the expressions above.

Call it what you want, La Place or No Place, its converting to s-domain.

$$V_i(s) = \frac{I1(s)}{sC1} + R1 \cdot I1(s) \quad \text{Eq 1}$$

$$E2(s) = \frac{I2(s)}{sC2} + R2 \cdot I2(s) \quad \text{Eq 2}$$

$$E1(s) = R1 \cdot I1(s) \quad \text{Eq 3}$$

$$V_o(s) = R2 \cdot I2(s) \quad \text{Eq 4}$$

METHOD 1:

This by building interconnected relationship, as I done in the past problems here.

The long way and the answer is same as the textbook answer.

If I had not done this then it may remain a mystery!

You may verify.

Method 2 is easy, which was my first re-action to the problem. Just place V_o/V_i , after forming their expression without the usual inter-related quations.

I will do method 2 after method 1 completion.

Rearrange Eq 1:

$$V_i(s) = I1(s) \cdot \left(\frac{1}{sC1} + R1 \right) \quad \text{Eq 5}$$

Rearrange Eq 2:

$$E2(s) = I2(s) \cdot \left(\frac{1}{sC2} + R2 \right) \quad \text{Eq 6}$$

Rearrange Eq 4:

$$I2(s) = \frac{V_o(s)}{R2} \quad \text{Eq 7...substitute in Eq 6}$$

$$E_2(s) = \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right) \quad \text{Eq 8}$$

$$E_2(s) = E_1(s): \quad E_1(s) = R_1 \cdot I_1(s) = E_2(s)$$

Next substitute $E_1(s)$ for $E_2(s)$ in Eq 8.

$$E_1(s) = E_2(s) = R_1 \cdot I_1(s) = \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right) \quad \text{Eq 9}$$

Substitute Eq 9 for $R_1 I_1(s)$ in Eq 1.

$$V_i(s) = \frac{I_1(s)}{sC_1} + \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right) \quad \text{Eq 10}$$

How do I substitute for $I_1(s)$, try Eq 5, then substitute into eq 10:

$$V_i(s) = I_1(s) \cdot \left(\frac{1}{sC_1} + R_1 \right) \quad \text{Eq 5}$$

$$I_1(s) = \frac{V_i(s)}{\left(\frac{1}{sC_1} + R_1 \right)} \quad \text{Eq 11.....substitute in Eq 10.}$$

$$V_i(s) = \frac{\frac{V_i(s)}{\left(\frac{1}{sC_1} + R_1 \right)}}{sC_1} + \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right) \quad \text{Eq 12...looks messy may do it.}$$

$$V_i(s) - \frac{V_i(s)}{sC_1} \cdot \left(\frac{1}{sC_1} + R_1 \right) = \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right)$$

$$V_i(s) - \frac{V_i(s)}{\left(\frac{1}{sC_1} + R_1 \right)} \cdot \frac{1}{sC_1} = \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right)$$

$$V_i(s) \cdot \left(1 - \frac{1}{\left(\frac{1}{sC_1} + R_1 \right) \cdot sC_1} \right) = \frac{V_o(s)}{R_2} \cdot \left(\frac{1}{sC_2} + R_2 \right)$$

$$V_i(s) \cdot \left(1 - \frac{1}{(1 + sC_1R_1)}\right) = V_o(s) \cdot \left(\frac{1}{sC_2R_2} + 1\right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\left(1 - \frac{1}{(1 + sC_1R_1)}\right)}{\left(\frac{1}{sC_2R_2} + 1\right)} \quad \text{Transfer function. Need simplifying.}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\left(\frac{(1 + sC_1R_1)}{(1 + sC_1R_1)} - \frac{1}{(1 + sC_1R_1)}\right)}{\left(\frac{1 + sC_2R_2}{sC_2R_2}\right)} = \frac{\left(\frac{(sC_1R_1)}{(1 + sC_1R_1)}\right)}{\left(\frac{1 + sC_2R_2}{sC_2R_2}\right)}$$

$$= \left(\frac{(sC_1R_1)}{(1 + sC_1R_1)}\right) \cdot \left(\frac{sC_2R_2}{1 + sC_2R_2}\right)$$

$$= \left(\frac{(s^2 \cdot C_1C_2R_1R_2)}{(1 + sC_2R_2 + sC_1R_1 + s^2 \cdot C_1C_2R_1R_2)}\right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{(s^2 \cdot C_1C_2R_1R_2)}{(1 + s(C_1R_1 + C_2R_2) + s^2 \cdot (C_1C_2R_1R_2))}$$

$$\text{Let } A = C_1C_2R_1R_2 \quad B = C_1R_1 \quad C = C_2R_2$$

$$\frac{V_o(s)}{V_i(s)} = \frac{(A \cdot s^2)}{(1 + (B + C) \cdot s + A \cdot s^2)} \quad \text{One Transfer Function - METHOD 1.}$$

$$C_1 := 1 \cdot 10^{-6} \quad C_2 := 0.5 \cdot 10^{-6} \quad R_1 := 1 \cdot 10^6 \quad R_2 := 1 \cdot 10^6$$

$$A := C_1 \cdot C_2 \cdot R_1 \cdot R_2 = 0.5 \quad \text{Or fraction: } \frac{1}{2} \quad B := C_1 \cdot R_1 + C_2 \cdot R_2 = 2$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\left(\frac{1}{2}\right) \cdot s^2}{1 + \left(\frac{3}{2}\right) \cdot s + \left(\frac{1}{2}\right) \cdot s^2} \quad \text{Multiply by 2.}$$

Non-Commercial Use Only

$$\frac{V_o(s)}{V_i(s)} = \frac{2 \left(\frac{1}{2} \right) \cdot s^2}{2 \cdot \left(1 + \left(\frac{3}{2} \right) \cdot s + \left(\frac{1}{2} \right) \cdot s^2 \right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{s^2}{2 + 3 \cdot s + s^2} = \frac{s^2}{s^2 + 3 \cdot s + 2} \quad \text{Answer. SAME AS TEXTBOOK!}$$

Calculate the output voltage, $t > 0$, for a unit step voltage input at $t=0$:

Since its unit step voltage input the initial conditions for $t < 0 = 0$.

So $i(-0) = i(0+ \dots \text{just near } 0) = 0$ and

$v(-0) = v(0+ \dots \text{just near } 0) = 0$ $v(++) = 1$

Comment: How do I get the numerator (zero) = 1 for $t > 0$ so the $V_i(s) = 1$ or greater; $u(t=0 \text{ or } t > 0) = 1$ or $u(t) = 1 \times \text{Constant}$. But NOT equal 0.

$$\frac{V_o(s)}{V_i(s)} = \frac{s^2}{(s+2)(s+1)} \quad V_o(s) = V_i(s) \cdot \frac{s^2}{(s+2)(s+1)}$$

$$V_o(s) = 1 \cdot \frac{s \cdot s}{(s+2)(s+1)} = \frac{A}{(s+2)} + \frac{B}{(s+1)}$$

To solve for coefficients using the? Method of proper fractions OR Equating coefficients of like powers.

$$s = A(s+1) + B(s+2) = As + A + Bs + 2B$$

$$s = s(A+B) + (A+2B)$$

Arrange for like terms:

$$s : s(A+B) \rightarrow A+B = 1 \quad \text{Eq 1}$$

$$0 : (A+2B) \rightarrow A+2B = 0 \quad \text{Eq 2}$$

$$B = -1 \quad \text{Eq 2-1}$$

Substitute B in Eq 1.

$$A+B = 1$$

$$A-1 = 1$$

$$A = 2$$

$$V_o(s) = \frac{A}{(s+2)} + \frac{B}{(s+1)} = \frac{2}{(s+2)} - \frac{1}{(s+1)}$$

Now with the coefficients, zeros, and poles I can form the voltage output in time domain. This will be an exponential equation because the voltage source is a step function, unity, or constant.

$$V_o(s) = Ae^{s1t} + Be^{s2t}$$

$$V_o(s) = -2e^{-2t} - 1e^{-1t}$$

Now to convert from s-domain to time domain:

$$v_o(t) = -2e^{-2t} - 1e^{-1t}$$

$$v_o(t) = -2e^{-2t} - e^{-t} \quad \text{Answer. Same as textbook.}$$

Please verify the solution steps and reasoning on the voltage output equation where $V_i(s) = 1$.

METHOD 2:

Now for Method 2, the supposed to be simpler and shorter solution.

$$V_i(s) = \frac{I1(s)}{sC1} + R1 \cdot I1(s) \quad \text{Eq 1}$$

$$E2(s) = \frac{I2(s)}{sC2} + R2 \cdot I2(s) \quad \text{Eq 2}$$

$$E1(s) = R1 \cdot I1(s) \quad \text{Eq 3}$$

$$V_o(s) = R2 \cdot I2(s) \quad \text{Eq 4}$$

Set up the transfer function, $V_o(s)/V_i(s)$ based on their respective equations directly:

$$\frac{V_o(s)}{V_i(s)} = \frac{R2 \cdot I2(s)}{\frac{I1(s)}{sC1} + R1 \cdot I1(s)} = \frac{I2(s) \cdot R2}{I1(s) \cdot \left(R1 + \frac{1}{sC1} \right)} \quad \text{Eq 5...maybe } I2(s) \text{ and } I1(s) \text{ substitution may help.}$$

$$I1(s) = \frac{E1(s)}{R1} \quad I2(s) = \frac{E2(s)}{\left(R2 + \frac{1}{sC2} \right)} \quad \text{From Eq 2 above.}$$

Non-Commercial Use Only

$$\frac{I_2(s)}{I_1(s)} = \frac{\frac{E_2(s)}{\left(R_2 + \frac{1}{sC_2}\right)}}{\frac{E_1(s)}{R_1}} = \frac{E_2(s)}{\left(R_2 + \frac{1}{sC_2}\right)} \cdot \frac{R_1}{E_1(s)}$$

Gain = 1, $E_2(s)/E_1(s) = 1$, therefore $E_1(s) = E_2(s)$.

$$E_1(s) = E_2(s)$$

Now the current ratio equation becomes:

$$\frac{I_2(s)}{I_1(s)} = \frac{R_1}{\left(R_2 + \frac{1}{sC_2}\right)}$$

Returning to Eq 5 substitute for $I_2(s)/I_1(s)$:

$$\frac{V_o(s)}{V_i(s)} = \frac{I_2(s) \cdot R_2}{I_1(s) \cdot \left(R_1 + \frac{1}{sC_1}\right)} \quad \text{Eq 5}$$

$$= \frac{R_1}{\left(R_2 + \frac{1}{sC_2}\right)} \cdot \frac{R_2}{\left(R_1 + \frac{1}{sC_1}\right)}$$

$$= \frac{R_1 R_2}{R_1 R_2 + \frac{R_2}{sC_1} + \frac{R_1}{sC_2} + \frac{1}{s^2 C_1 C_2}}$$

Let: $A = R_1 \cdot R_2 = 1 \cdot 10^{12}$

$$B = \frac{R_2}{C_1} = 1 \cdot 10^{12} \quad C = \frac{R_1}{C_2} = 2 \cdot 10^{12}$$

$$D = \frac{1}{C_1 \cdot C_2} = 2 \cdot 10^{12}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1 \cdot 10^{12}}{1 \cdot 10^{12} + \frac{1 \cdot 10^{12}}{s} + \frac{2 \cdot 10^{12}}{s} + \frac{2 \cdot 10^{12}}{s^2}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + \frac{1}{s} + \frac{2}{s} + \frac{2}{s^2}} = \frac{1}{1 + \frac{3}{s} + \frac{2}{s^2}}$$

Multiply by s^2
top and bottom.

Chapter 6 Part C. Solving Problems (Examples and Exercises). Source of study material: 1). Electric Circuits 6th Ed Schaums - Nahvi & Edminister. 2). Solutions & Problems of Control System - AK Jairath. 3). Engineering Circuits Analysis - Hyat & Kemmerly. My Homework. This is a pre-requisite study for Laplace Transforms in circuit analysis. Karl S. Bogha.

$$\frac{V_o(s)}{V_i(s)} = \frac{(s^2) \cdot 1}{(s^2) \cdot \left(1 + \frac{3}{s} + \frac{2}{s^2}\right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{s^2}{s^2 + 3s + 2}$$


Answer.

Same method used by engineer the faster method.

The short method may give the impression there is no relationship with the components like that established in the longer method. However, the transfer function's definition is just that, output divided by input. Do consider the circuit's components and connections, and carefully construct the equations.

The remaining part on the output voltage same as completed following the long method of the transfer functions.

Chp 1 Problem 1.13:

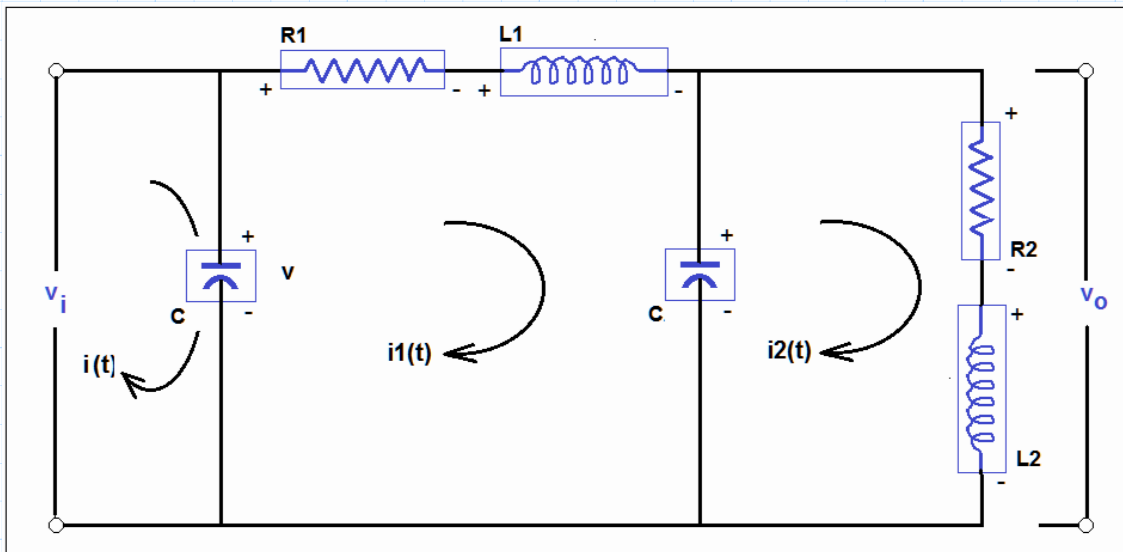


Determine the transfer function of the electrical network above:

Solution:

$C_1 = C_2$, the question did not show C_1 and C_2 , rather C .

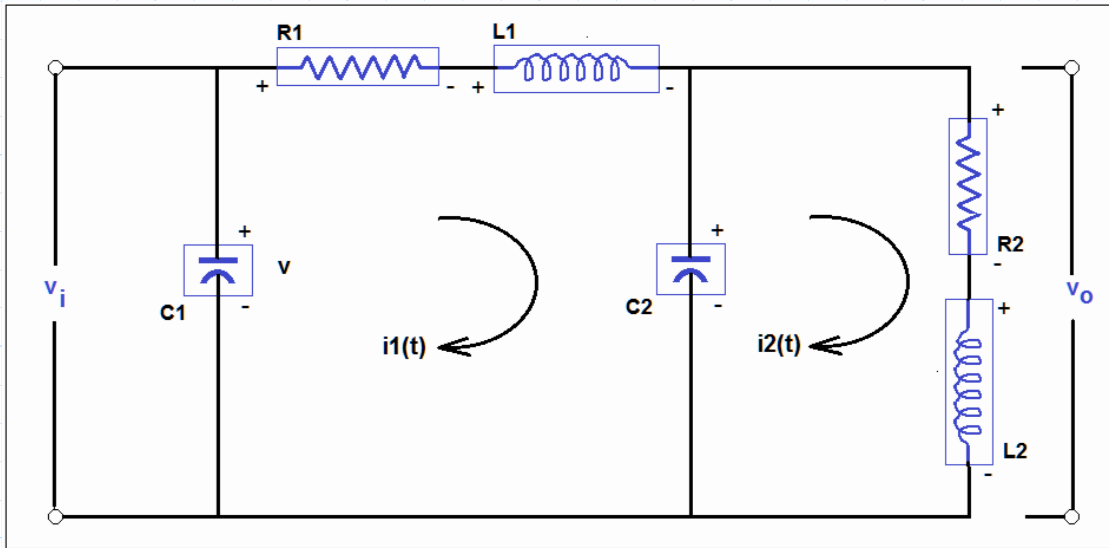To ease tracking the solution they were made into C_1 and C_2 .



The basic steps we first started with provided here again, these steps were much the same to what we did in the previous problems.

The **steps involved** in obtaining the transfer function are:

1. Write differential equations of the system.
2. Replace terms involving $\frac{d}{dt}$ by s and $\int dt$ by $1/s$, for inductor and capacitor respectively.
3. Eliminate all but the desired variable.

Step 1:

Check current flow direction. Coming out of C_1 -ve terminal -ve voltage.

$v_i(t)$:

$$v_i(t) = -\frac{1}{C_1} \cdot \int i(t) dt$$

Check current flow direction. Coming out of C_1 -ve terminal -ve voltage (left loop).

$$\frac{1}{C_1} \cdot \int (i_1(t) - i(t)) dt = \frac{1}{C_1} \cdot \int i_1(t) dt - v_i(t)$$

This can be written as:

$$v_i(t) + \frac{1}{C_1} \cdot \int i_1(t) dt = 0$$

Sum of voltages, next $v_i(t)$ to the LHS, resulting in the same.

$$-v_i(t) = \frac{1}{C_1} \cdot \int i_1(t) dt \quad \text{OR} \quad v_i(t) = -\frac{1}{C_1} \cdot \int i_1(t) dt$$

Step 1:

$v_i(t)$:

$$v_i(t) = -\frac{1}{C_1} \cdot \int i(t) dt \quad \text{Check current flow direction. Coming out of } C_1 \text{ -ve terminal -ve voltage.}$$

$$v_i(t) = \frac{1}{C_1} \cdot \int i_1(t) dt \quad \text{Check current flow direction. Coming out of } C_1 \text{ -ve terminal -ve voltage.}$$

This can be written as:

$$v_i(t) + \frac{1}{C_1} \cdot \int i_1(t) dt = 0 \quad \text{Sum of voltages, next } v_i(t) \text{ to the LHS, resulting in the same.}$$

$$-v_i(t) = \frac{1}{C_1} \cdot \int i_1(t) dt \quad \text{OR} \quad v_i(t) = -\frac{1}{C_1} \cdot \int i_1(t) dt$$

Centre loop:

$$0 = \frac{1}{C_1} \cdot \int i_1(t) dt + R_1 i_1(t) + L_1 \left(\frac{di_1(t)}{dt} \right) + \frac{1}{C_2} \cdot \int (i_1(t) - i_2(t)) dt$$

$$-v_i(t) = \frac{1}{C_1} \cdot \int i_1(t) dt \quad \text{Substitute in equation above.}$$

$$0 = -v_i(t) + R_1 i_1(t) + L_1 \left(\frac{di_1(t)}{dt} \right) + \frac{1}{C_2} \cdot \int (i_1(t) - i_2(t)) dt$$

$$v_i(t) = R_1 i_1(t) + L_1 \left(\frac{di_1(t)}{dt} \right) + \frac{1}{C_2} \cdot \int (i_1(t) - i_2(t)) dt \quad \text{Eq 1}$$

$v_o(t)$:

$$v_o(t) = R_2 \cdot i_2(t) + L_2 \left(\frac{di_2}{dt} \right) \quad \text{Eq 2}$$

Non-Commercial Use Only

Right loop:

$$0 = \frac{1}{C2} \cdot \int (i2(t) - i1(t)) dt + R2i2(t) + L2 \left(\frac{di2(t)}{dt} \right) \quad \text{Eq 3}$$

Substitute $v_o(t)$ into Right Loop.

Step 2:

Assuming all initial conditions for L and C are zero.

We proceed with taking the? *Laplace Transform*. Convert to s-domain.

$$v_i(t) = R1i1(t) + L1 \left(\frac{di1(t)}{dt} \right) + \frac{1}{C2} \cdot \int (i1(t) - i2(t)) dt \quad \text{Eq 1}$$

$$V_i(s) = R1I1(s) + sL1 I1(s) + \frac{1}{sC2} \cdot (I1(s) - I2(s))$$

$$V_i(s) = R1I1(s) + sL1 I1(s) + \frac{1}{sC2} \cdot (I1(s) - I2(s)) \quad \text{Eq 4 <---Same as textbook.}$$

$$v_o(t) = R2 \cdot i2(t) + L2 \left(\frac{di2}{dt} \right) \quad \text{Eq 2}$$

$$V_o(t) = R2 \cdot I2(s) + sL2I2(s) \quad \text{Eq 5 <----Same as textbook.}$$

$$0 = \frac{1}{C2} \cdot \int (i2(t) - i1(t)) dt + R2i2(t) + L2 \left(\frac{di2(t)}{dt} \right) \quad \text{Eq 3}$$

$$0 = \frac{1}{sC2} (I2(s) - I1(s)) + R2I2(s) + sL2 \cdot I2(s) \quad \text{Eq 6}$$

Step 3:

$$\frac{V_o(t)}{V_i(s)} = \frac{R2 \cdot I2(s) + sL2I2(s)}{R1I1(s) + sL1 I1(s) + \frac{1}{sC2} \cdot (I1(s) - I2(s))}$$

Same as textbook.

Past this point you have to solve it for the best possible form.

$$\frac{V_o(t)}{V_i(s)} = \frac{I2(s) \cdot (R2 + sL2)}{I1(s) \cdot \left(R1 + sL1 + \frac{1}{sC2} \right) - \frac{1}{sC2} I2(s)}$$

Find a substitute for I_2 in terms of I_1 for the denominator.

$$0 = \frac{1}{sC_2} (I_2(s) - I_1(s)) + R_2 I_2(s) + sL_2 \cdot I_2(s) \quad \text{Eq 6}$$

Solve for I_2 above:

$$\frac{1}{sC_2} I_2(s) + R_2 I_2(s) + sL_2 \cdot I_2(s) = \frac{I_1(s)}{sC_2} \quad \text{Multiply by } sC_2.$$

$$I_2(s) + R_2 I_2(s) sC_2 + sL_2 \cdot I_2(s) sC_2 = I_1(s)$$

$$I_2(s) \cdot (1 + sC_2 R_2 + s^2 C_2 L_2) = I_1(s) \quad \text{Eq 7}$$

$$I_2(s) = \frac{I_1(s)}{(1 + sC_2 R_2 + s^2 C_2 L_2)}$$

$$\frac{V_o(t)}{V_i(s)} = \frac{I_2(s) \cdot (R_2 + sL_2)}{I_1(s) \cdot \left(R_1 + sL_1 + \frac{1}{sC_2} \right) - \frac{1}{sC_2} I_2(s)}$$

Substitute $I_2(s)$ in denominator above.

$$\frac{V_o(t)}{V_i(s)} = \frac{I_2(s) \cdot (R_2 + sL_2)}{I_1(s) \cdot \left(R_1 + sL_1 + \frac{1}{sC_2} \right) - \frac{1}{sC_2} \cdot \frac{I_1(s)}{(1 + sC_2 R_2 + s^2 C_2 L_2)}}$$

$$\frac{V_o(t)}{V_i(s)} = \frac{I_2(s) \cdot (R_2 + sL_2)}{I_1(s) \cdot \left(\left(R_1 + sL_1 + \frac{1}{sC_2} \right) - \left(\frac{1}{sC_2 + s^2 C_2^2 R_2 + s^3 C_2^2 L_2} \right) \right)}$$

$$\frac{V_o(t)}{V_i(s)} = \left(\frac{I_2(s)}{I_1(s)} \right) \cdot \frac{(R_2 + sL_2)}{\left(R_1 + sL_1 + \frac{1}{sC_2} \right) - \left(\frac{1}{sC_2 + s^2 C_2^2 R_2 + s^3 C_2^2 L_2} \right)}$$

Find an equation for $I_2(s)/I_1(s)$ Eq 7 below.

$$I_2(s) \cdot (1 + sC_2 R_2 + s^2 C_2 L_2) = I_1(s) \quad \text{Eq 7}$$

$$\frac{I_2(s)}{I_1(s)} = \frac{1}{(1 + sC_2R_2 + s^2 C_2L_2)}$$

Substitute $\frac{I_2(s)}{I_1(s)}$ in transfer function

$$\frac{V_o(t)}{V_i(s)} = \left(\frac{1}{1 + sC_2R_2 + s^2 C_2L_2} \right) \left(\frac{(R_2 + sL_2)}{\left(R_1 + sL_1 + \frac{1}{sC_2} \right) - \left(\frac{1}{sC_2 + s^2 C_2^2 R_2 + s^3 C_2^2 L_2} \right)} \right)$$

$$\frac{V_o(t)}{V_i(s)} = \frac{(R_2 + sL_2)}{(1 + sC_2R_2 + s^2 C_2L_2) \cdot \left(R_1 + sL_1 + \frac{1}{sC_2} \right) - \left(\frac{(1 + sC_2R_2 + s^2 C_2L_2)}{sC_2(1 + sC_2R_2 + s^2 C_2L_2)} \right)}$$

Set $C_1 = C_2 = C$, as given.

$$\frac{V_o(t)}{V_i(s)} = \frac{(R_2 + sL_2)}{(1 + sCR_2 + s^2 CL_2) \cdot \left(R_1 + sL_1 + \frac{1}{sC} \right) - \left(\frac{1}{sC} \right)}$$

Expand the left side terms at the bottom, and set equal to A.
Then the bottom right side term's denominator set to B.

$$(1 + sCR_2 + s^2 CL_2) \cdot \left(R_1 + sL_1 + \frac{1}{sC} \right) =$$

$$R_1 + sL_1 + \frac{1}{sC} + sCR_1R_2 + s^2 CR_2L_1 + R_2 + s^2 CR_1L_2 + s^3 CL_1L_2 + sL_2 = A$$

$$s^3 (CL_1L_2) + s^2 \cdot (CR_2L_1 + CR_1L_2) + s \left(L_1 + \frac{1}{s^2 C} + CR_1R_2 + L_2 \right) + (R_1 + R_2) = A$$

$$s^3 (L_1L_2) + s^2 \cdot C (R_2L_1 + R_1L_2) + s \left(L_1 + L_2 + CR_1R_2 + \frac{1}{s^2 C} \right) + (R_1 + R_2) = A$$

$$\frac{1}{sC} = B$$

Non-Commercial Use Only

Chapter 6 Part C. Solving Problems (Examples and Exercises). Source of study material: 1). Electric Circuits 6th Ed Schaums - Nahvi & Edminister. 2). Solutions & Problems of Control System - AK Jairath. 3). Engineering Circuits Analysis - Hyat & Kemmerly. My Homework. This is a pre-requisite study for Laplace Transforms in circuit analysis. Karl S. Bogha.

$$\frac{V_o(t)}{V_i(s)} = \frac{(R2 + sL2)}{A - \left(\frac{1}{B}\right)}$$

$$s^3 (L1L2) + s^2 \cdot C (R2L1 + R1L2) + s \left(L1 + L2 + CR1R2 + \frac{1}{s^2 C} \right) + (R1 + R2) = A$$

In my equation above there is $(1/s^2C)$ this is not in the textbook answer. Textbook answer below does not have B term $(1/sC)$ maybe this was negligible to the overall function because it becomes huge in the denominator, and when it divides the numerator it's small or negligible. Usually C is in microFarad units. This may also be the case for $(1/s^2C)$ in the A term. Except for this my result is the same.

$$\frac{V_o(t)}{V_i(s)} = \frac{R2 + sL2}{s^3 (L1L2) + s^2 \cdot C (R2L1 + R1L2) + s \left(L1 + L2 + CR1R2 + \frac{1}{s^2 C} \right) + (R1 + R2) - \left(\frac{1}{sC} \right)}$$

Neglecting $(1/sC)$ and $(1/s^2 C)$:

$$\frac{V_o(t)}{V_i(s)} = \frac{R2 + sL2}{s^3 (L1L2) + s^2 \cdot C (R2L1 + R1L2) + s (L1 + L2 + CR1R2) + (R1 + R2)}$$

My Answer.

You can verify this answer correct it, or present your own. *Here this is as far as I am going.*

Textbook **Answer:**

$$\frac{V_o(s)}{V_i(s)} = \frac{R2 + sL2}{s^3 CL1L2 + s^2 C (R1L2 + L1R2) + s (L1 + L2 + CR1R2) + (R1 + R2)}$$

Transfer function above does look tidy!
You solve it for yourself if you see a need.

You can sort it with your local lecturer/engineer.
Apologies for any errors and omissions.

This brings to end the 13 example problems.
Next Schaum's Chapter 8 Solved Problems.